

Phase detector and Phase locked loop

Hersh Aditya Samdani (EP22B027)

Aim:

- To study the workings of Phase Detector and Phase Locked Loop by constructing a phase detector and phase-locked loop
- To find the variation of phase difference with potentiometer resistance, and output DC.
- To study the relationship between Phase Difference and the DC control signal of PLL.
- Calculate the lock range and the capture range for different capacitor values.

Apparatus:

- IC565 Op-Amp
- DC Power Supply
- Oscilloscope
- Function Generator
- Multimeter
- 10K Potentiometer
- Resistors and Capacitors of required values

Setup:

Observations:

$$V_{pp} = 12V, f = 5kHz$$

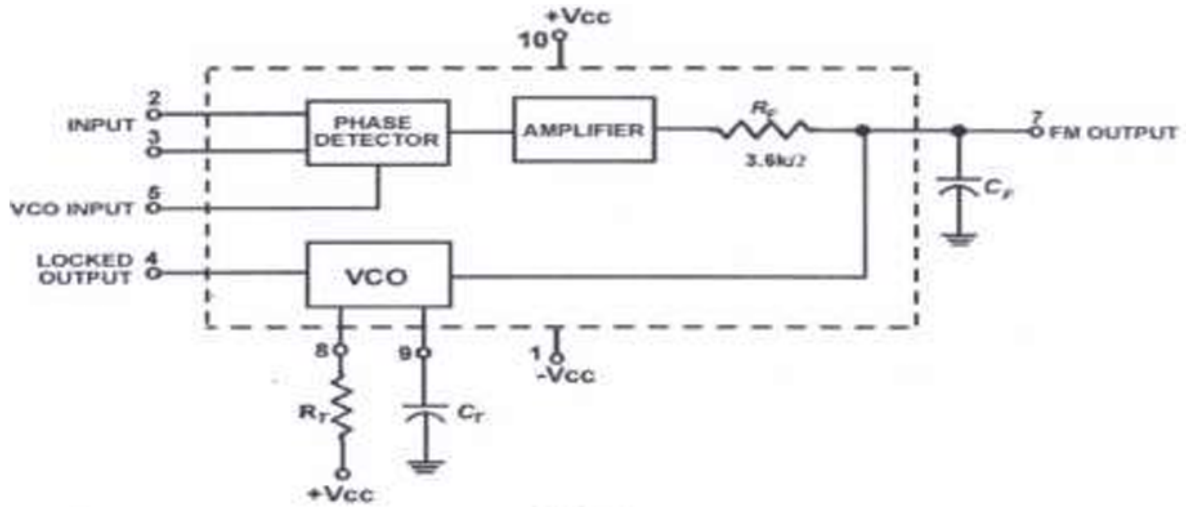


Figure 1: Block Diagram of PLL-565

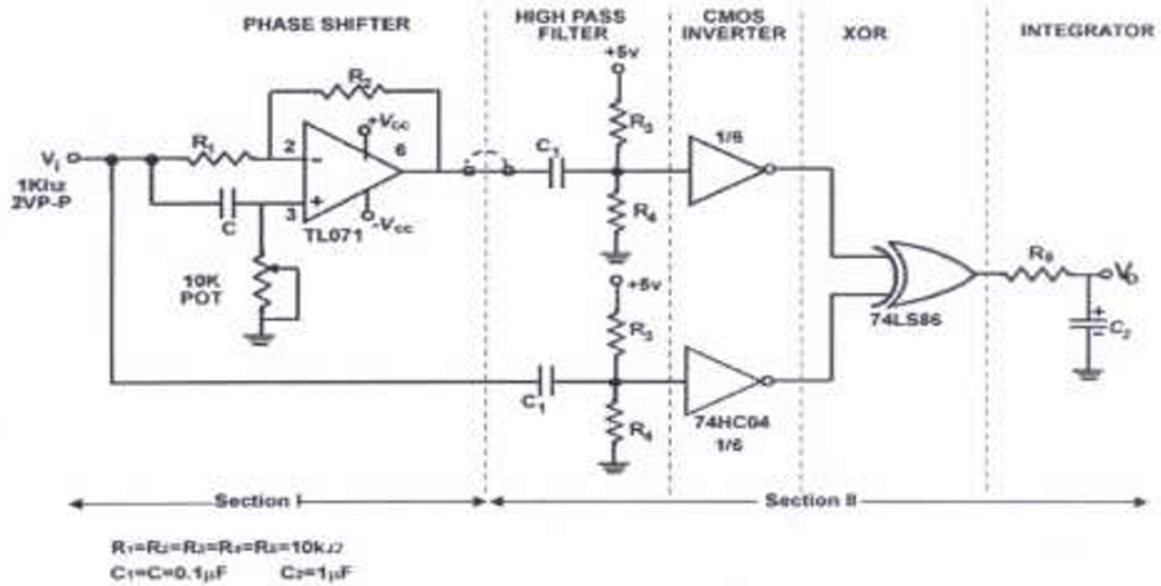


Figure 2: Circuit Diagram of Phase Shifter

 


Figure 3: Experimental PLL Circuit

| Sl. No | Resistance (in k Ω) | Phase Difference φ (in $^{\circ}$) |
|--------|-----------------------------|---|
| 1 | 0.0063 | 180 |
| 2 | 0.0566 | 170 |
| 3 | 0.1018 | 160 |
| 4 | 0.155 | 150 |
| 5 | 0.2112 | 140 |
| 6 | 0.2725 | 130 |
| 7 | 0.342 | 120 |
| 8 | 0.418 | 110 |
| 9 | 0.507 | 100 |
| 10 | 0.591 | 90 |
| 11 | 0.683 | 80 |
| 12 | 0.806 | 70 |
| 13 | 0.919 | 60 |
| 14 | 1.180 | 50 |
| 15 | 1.472 | 40 |
| 16 | 1.898 | 30 |
| 17 | 2.898 | 20 |
| 18 | 6.5 | 10 |

Table 1: Variation of Phase Difference with Resistance



Figure 4: Plot of Phase Difference vs Resistance

| Sl.No | C_f (in μF) | f_{\max} (kHz) | f_{\min} (kHz) | B_c (kHz) |
|-------|---------------------------|------------------|------------------|-------------|
| 1 | 0.1 | 6.0 | 3.2 | 2.8 |
| 2 | 0.2 | 6.5 | 2.7 | 3.8 |
| 3 | 0.047 | 7.0 | 2.7 | 4.3 |

Table 2: Capture Range Data

| Sl.No | Frequency (kHz) | Voltage (V) |
|-------|-----------------|-------------|
| 1 | 4 | 9.24 |
| 2 | 5 | 8.53 |
| 3 | 6 | 8.88 |

Table 3: FM Output Readings

Error Analysis:

- Error in Resistance (ΔR) = 0.1 kHz
- Error in Phase Difference ($\Delta\phi$) = 1°
- Error in Voltage (ΔV) = 0.001 V

Error in Capture Range:

- $\Delta f_{min} = 0.01\text{kHz}$
- $\Delta f_{max} = 0.01\text{kHz}$
- Error in measuring $\Delta B_c = \Delta f_{min} + \Delta f_{max} = 0.02\text{kHz}$
- For $C_f = 0.1\mu\text{F}$, $B_c = 2.8 \pm 0.02\text{kHz}$
- For $C_f = 0.2\mu\text{F}$, $B_c = 3.8 \pm 0.02\text{kHz}$
- For $C_f = 0.047\mu\text{F}$, $B_c = 4.3 \pm 0.02\text{kHz}$

Results:

- Phase difference between input and output voltage and resistance is nearly linear decreasing but decays with increase in resistance.
- The control DC voltage from the phase detector seemingly decreases with decrease in the phase difference in an almost linear relationship.
- We can see the capture range always falls within the lock in range and decreases with increase in the capacitance value.
- The FM output voltage decreases with increase in input frequency.

Discussion:

- We can thus see the use of phase locked loops for clock generation and synchronization in digital systems. Through it, we obtain stable and precise timing across various components.
- We can generate higher frequency clocks from a low frequency reference using frequency multipliers, which find use in microprocessors and communication systems.
- The nonlinear nature of the FM output voltage trend with input frequency demonstrates the filtering and demodulation behavior of the loop filter and VCO.

- By tuning the capacitor C_f , we directly influenced the capture range, which demonstrates how loop dynamics depend on component selection—this is important for real-world applications like data recovery in noisy conditions.